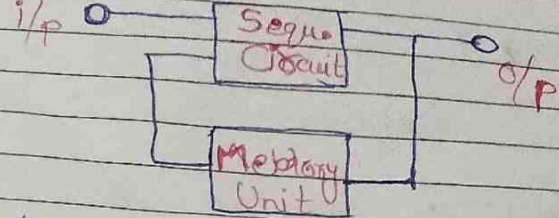


UNIT - 4  
"SEQUENTIAL CIRCUIT"

Page No.:

★ Sequential circuit -



★ Combinational Circuit -



Assignment Ques.


Que. 1 Write the difference b/w sequential & combination circuit.

Que. 2 Describe clocked R.S Flip-flop.

Que. 3 Write a short note on Race around condition.

Que. 4 Same → analysis of T flip-flop.

State diagram  
 bhí brang  
 hai

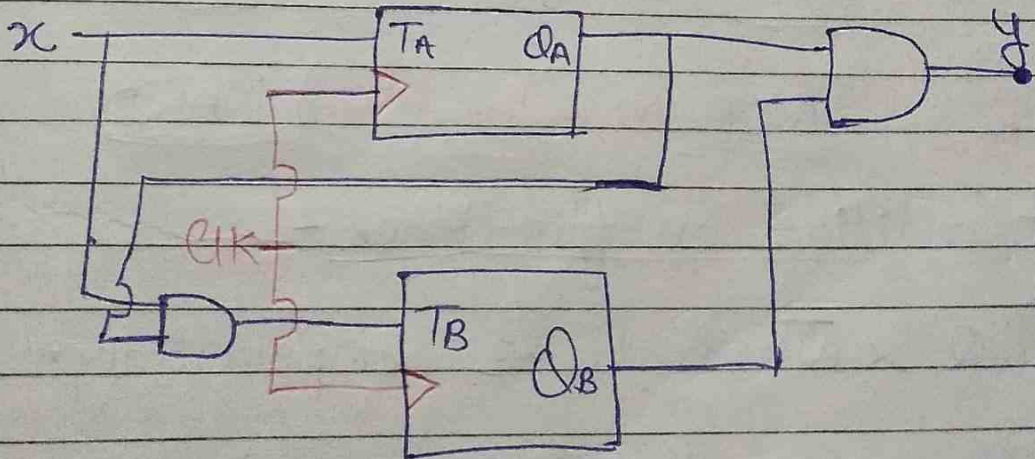

NEW STARTED


Chapter - 4  
Sequential Circuit

Date 24.01.23 Page No. \_\_\_\_\_

★ SR Latch with NOR Gate

NOR

0	0	1
0	1	0
1	0	0
1	1	0

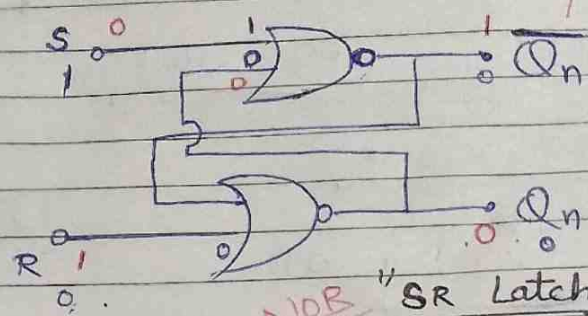

Don't change

$$\left( \begin{array}{l} S \rightarrow \overline{Q} \\ R \rightarrow Q \end{array} \right)$$


NOR SR Latch Table

S	R	Q <sub>n</sub>
0	0	Last value
0	1	0
1	0	1
1	1	Invalid

★ SR Latch with NAND Gate

NAND

0	0	1
0	1	1
1	0	1
1	1	0

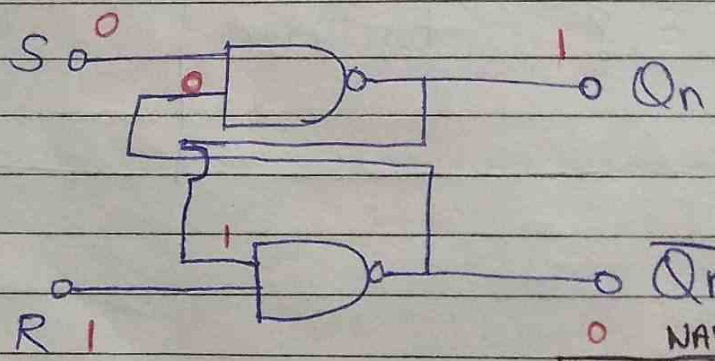

$$\left( \begin{array}{l} S \rightarrow Q_n \\ R \rightarrow \overline{Q_n} \end{array} \right)$$

$$\left( X = \begin{array}{l} \text{Invalid} \\ \text{Last} \\ \text{Value} \end{array} \right)$$

NAND Latch


S	R	Q <sub>n</sub>
0	0	Invalid
0	1	1
1	0	0
1	1	Last value

TRUTH TABLE SAME Hai

Date: / / Page No.:

★ SR FlipFlop with NAND Latch, -

NAND		
0	0	1
0	1	1
1	0	1
1	1	0

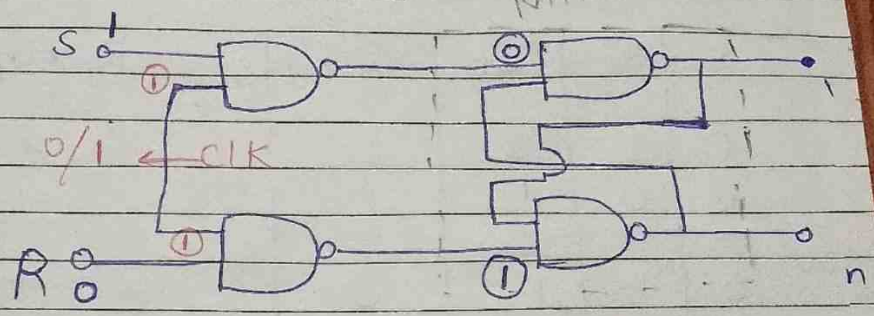


NAND Batch		
0	0	Invalid
0	1	1
1	0	0
1	1	last value

Truth Table	CLK	S	R	Qn
	0	X	X	Qn
	1	0	0	last value
	1	0	1	0
	1	1	0	1
	1	1	1	X

★ SR FlipFlop with NOR Latch, -

AND		
0	0	0
0	1	0
1	0	0
1	1	1

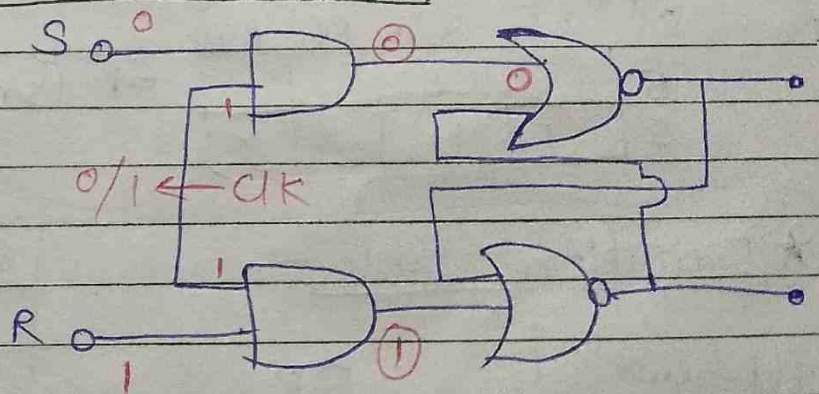


NOR Latch		
S	R	Qn
0	0	Last Value
0	1	0
1	0	1
1	1	Invalid

Same Truth Table!

★ Characteristic Table -

S	R	Q <sub>n</sub>	Q <sub>n+1</sub>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	Invalid
1	1	1	Invalid

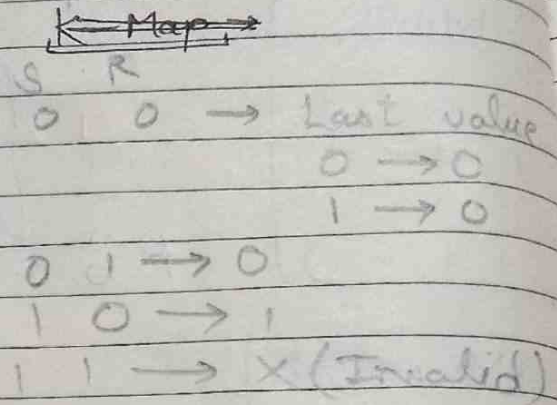

No Use Indirectly

▶ K-Map -

S \ RQ <sub>n</sub>	$\bar{R}\bar{Q}_n$	$\bar{R}Q_n$	$R\bar{Q}_n$	$RQ_n$
$\bar{S}$		1		
S	1	1	X	X

$\Rightarrow Q_{n+1} = \underline{S + \bar{R}Q_n}$

★ Excitation Table -

Reference  
Character  
Table  
of Q<sub>n</sub>, Q<sub>n+1</sub>


SR  
Flip Flop  
with NAND  
(OR)  
NOR Latch

Q <sub>n</sub>	Q <sub>n+1</sub>	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

★ JK FlipFlop -

"TRUTH TABLE"

J	K	Q <sub>n</sub>
0	0	Last value
0	1	0
1	0	1
1	1	$\overline{Q_n}$

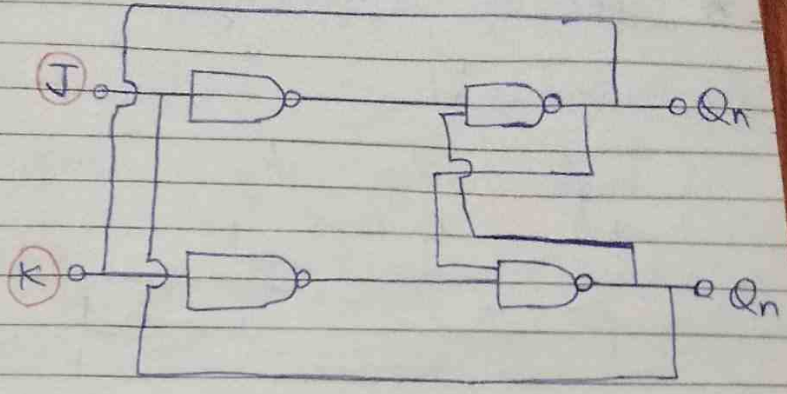

"Characteristic Table"


J	K	Q <sub>n</sub>	Q <sub>n+1</sub>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

"Excitation Table"

Q <sub>n</sub>	Q <sub>n+1</sub>	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0




	$\overline{KQ_n}$	$\overline{KQ_n}$	$\overline{KQ_n}$	$\overline{KQ_n}$
$\overline{J}$		1		
J	1	1		1

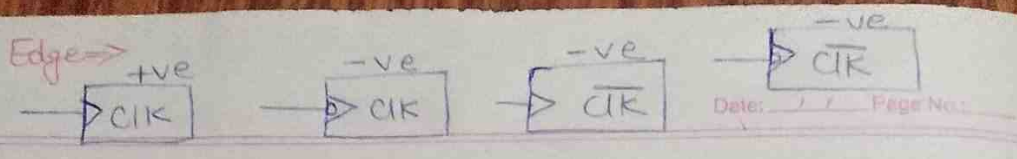$Q_{n+1} = \overline{KQ_n} + J\overline{Q_n}$



★ Types of Triggering -

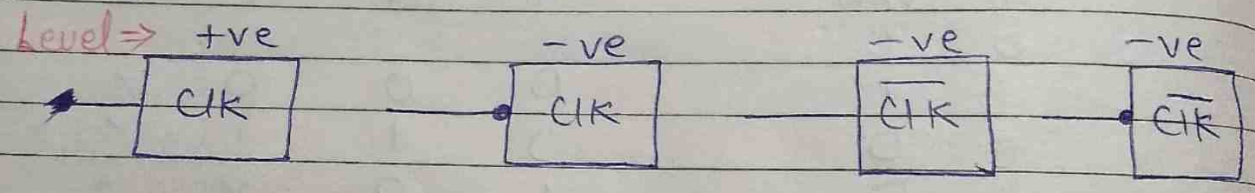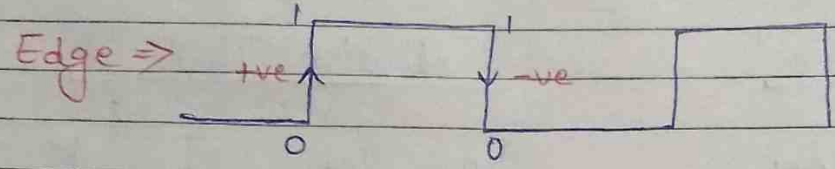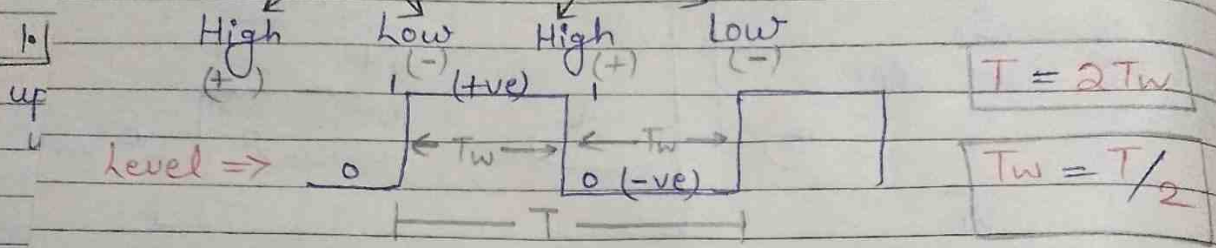(for Moretime) Level  $\swarrow$   $\searrow$  Edge (at instant)




★ Race Around Condition -

- ① Level Triggered
- ②  $J=K=1$  (Toggle)
- ③  $T_w \gg T_d$  (Time taken by flip-flop in proceed)

All three should happen  
at same Time!

★ Master Slave flip-flop -

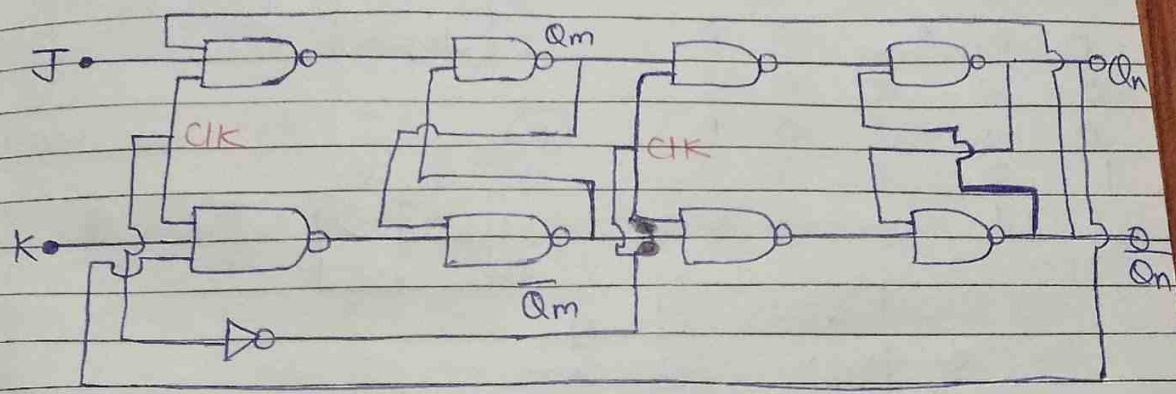

Convert → SR → D

Characteristic Table of D

D	$Q_n$	$Q_{n+1}$
0	0	0
0	1	0
1	0	1
1	1	1

Excitation Table of SR

$Q_n$	$Q_{n+1}$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

- ▶ Step:1 - Charac. Table of D (Required)
- ▶ Step:2 - Excitation Table of SR (Required)
- ▶ Step:3 - Merge
- ▶ Step:4 - K-Map of S & R.
- ▶ Step:5 - Block Diagram.

★ Merge -

D	Q <sub>n</sub>	Q <sub>n+1</sub>	S	R
0	0	0	0	X
0	1	0	0	1
1	0	1	1	0
1	1	1	X	0

Ⓢ


D	Q <sub>n</sub>	Q <sub>n</sub>	Q <sub>n</sub>
0	0	0	0
0	1	0	X

S = D

Ⓡ

D	Q <sub>n</sub>	Q <sub>n</sub>	Q <sub>n</sub>
0	0	0	0
0	1	X	X

R = D̄

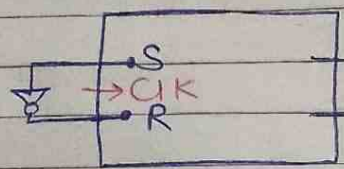

← Block Diagram

• Convert SR → T -

"Charac. Table of T"

"Excitation of SR"

T	Q <sub>n</sub>	Q <sub>n+1</sub>
0	0	0
0	1	1
1	0	1
1	1	0

Q <sub>n</sub>	Q <sub>n+1</sub>	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

★ Merge -

T	Q <sub>n</sub>	Q <sub>n+1</sub>	S	R
0	0	0	0	X
0	1	1	X	0
1	0	1	1	0
1	1	0	0	1

Ⓢ

T	Q <sub>n</sub>	Q <sub>n</sub>	Q <sub>n</sub>
0	0	0	0
0	1	0	K
1	0	1	0

S = TQ̄<sub>n</sub>

Ⓡ

T	Q <sub>n</sub>	Q <sub>n</sub>	Q <sub>n</sub>
0	0	0	0
0	1	X	0
1	0	0	1

R = TQ<sub>n</sub>



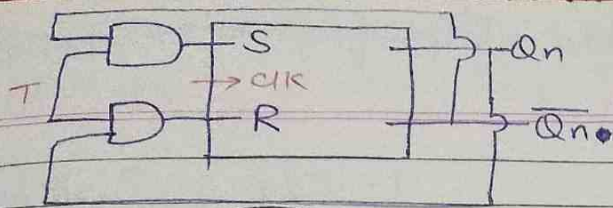


Diagram of previous Page  
Date: / /

★ Convert SR → JK -

"Charac. Table of JK"

"Excitation Table of S.R"

J	K	$Q_n$	$Q_{n+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$Q_n$	$Q_{n+1}$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

(S)

J	$\bar{K}Q_n$	$\bar{K}Q_n$	$\bar{K}Q_n$	$\bar{K}Q_n$
$\bar{J}$		X		
J	1	X		1

$S = JQ_n$


★ Merge -

J	K	$Q_n$	$Q_{n+1}$	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

(R)

J	$\bar{K}Q_n$	$\bar{K}Q_n$	$\bar{K}Q_n$	$\bar{K}Q_n$
$\bar{J}$	X		1	X
J			1	

$R = KQ_n$

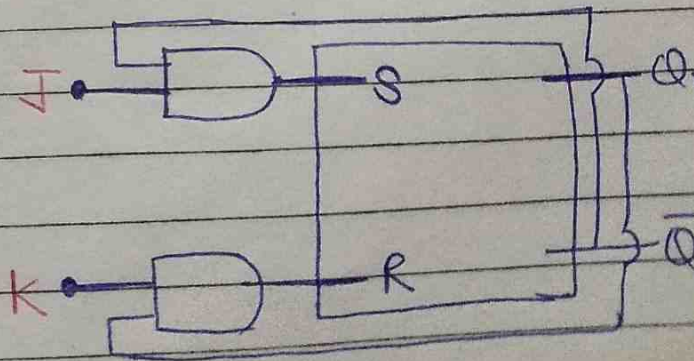

[ Register mai D flip-flop use hota hai ]

Date: / / Page No: \_\_\_\_\_

★ Register -


Left shift      Right shift

(×)

(÷)

Multiple	Division
0001	1000
0010	0100
0100	0010
1000	0001

★ SISO - (Serial Input Serial Output)

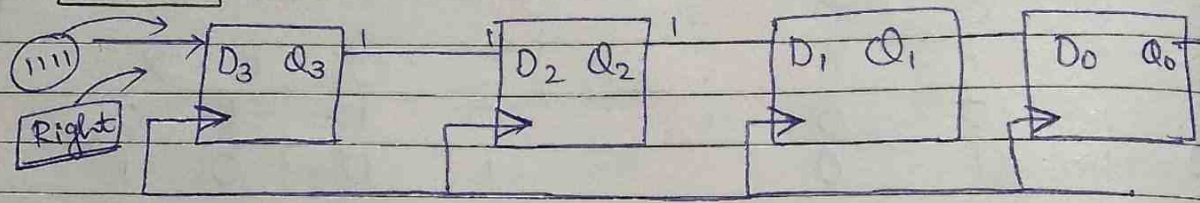

CLK	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
1	0	0	0	1	0	0	0	1
2	0	0	1	1	0	0	1	1
3	0	1	1	1	0	1	0	0
4	1	1	1	1	1	1	1	1



CLK<sub>5</sub>  
+3  
n-1

Jitne bit hote hai utni hi bits lagti hai  
 4bit = 4bit  
 nbit = nbit

SIso  
mai

Date: / / Page No.:

★ D Flip-flop :-

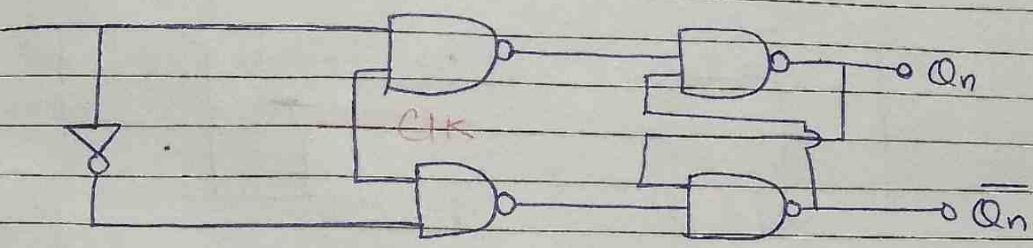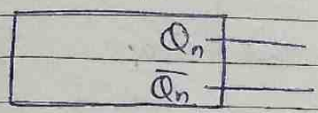

● Characteristic Table -

● Excitation Table -


D	$Q_n$	$Q_{n+1}$
0	0	0
0	1	0
1	0	1
1	1	1

$Q_n$	$Q_{n+1}$	D
0	0	0
0	1	0
1	0	1
1	1	1


Character. eq.  $\Rightarrow Q_{n+1} = D$

(Toggle flip-flop) (Same value pr change nhi hata)

★ T → flip-flop -

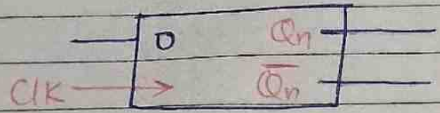

T	Qn
0	Qn
1	$\bar{Q}_n$

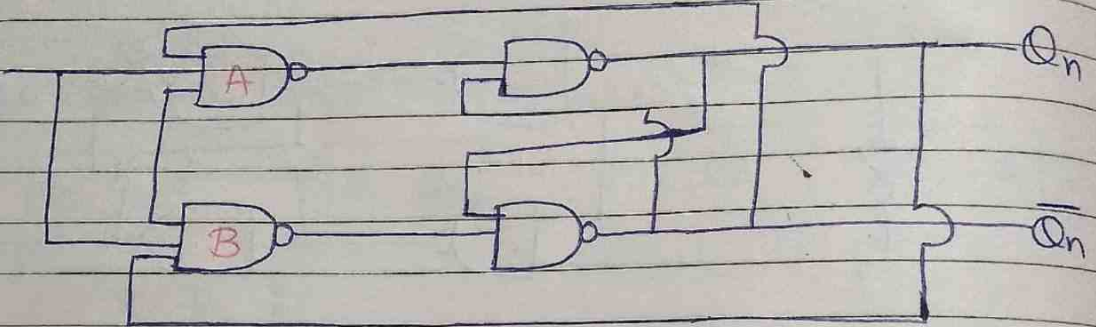

★ Characteristic Table -

★ Excitation Table -

T	Qn	Qn+1
0	0	0
0	1	1
1	0	1
1	1	0

Qn	Qn+1	T
0	0	0
0	1	1
1	0	1
1	1	0

★  $Q_{n+1} = T\bar{Q}_n + Q_n\bar{T}$


S = Serial  
P = Parallel

"Charac. Table Samj lo"

Date: / / Page No:

★ Register


① SIPO

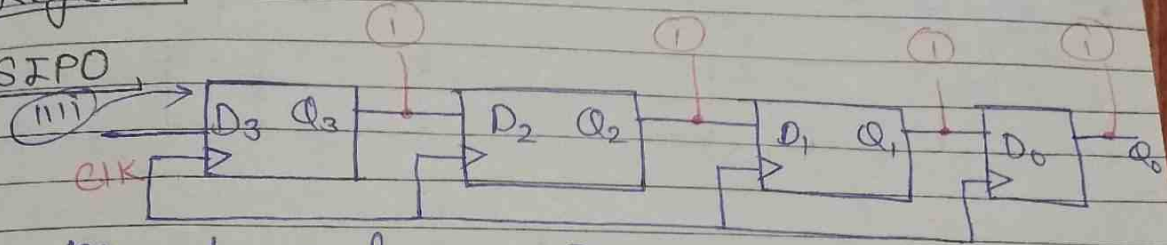

no. of cycle = 0

CLK	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
1	0	0	0	1	0	0	0	1
2	0	0	1	1	0	0	1	1
3	0	1	1	1	0	1	1	1
4	1	1	1	1	1	1	1	1

② PISO -

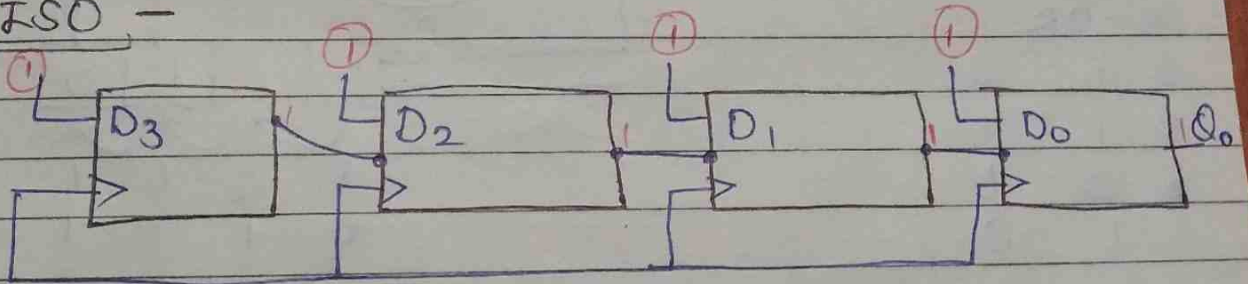


no. of cycle required = n-1

CLK	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
①	1	1	1	1	1	1	1	1


Que in Paper (Flip-flop, register, conversion)

Date: \_\_\_\_\_ Page No.: \_\_\_\_\_

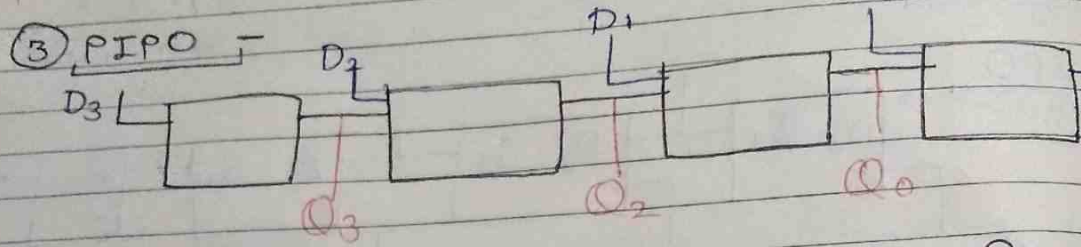

CK	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
1	1	1	1	1	1	1	1	1

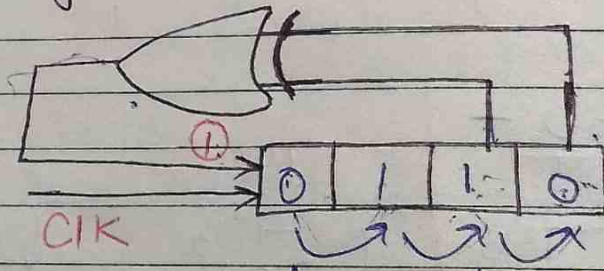Que In a 4 bit right-shift register how many clock pulses are required to change the content of register all 1.



X-OR

0	0	0
0	1	1
1	0	1
1	1	0

6 Ans.

CK <sub>1</sub>	1	0	1	1
CK <sub>2</sub>	0	1	0	1
CK <sub>3</sub>	1	0	1	0
CK <sub>4</sub>	1	1	0	1
CK <sub>5</sub>	1	1	1	0
CK <sub>6</sub>	1	1	1	1


M.F.★  
 ★★★★★ "Confirm"  
 6 marks Que in exam

Hold mai Jo value phle  
 hai vahi rahegi

★ Analysis of sequential circuit -

● Analysis of D-Flip-Flop -

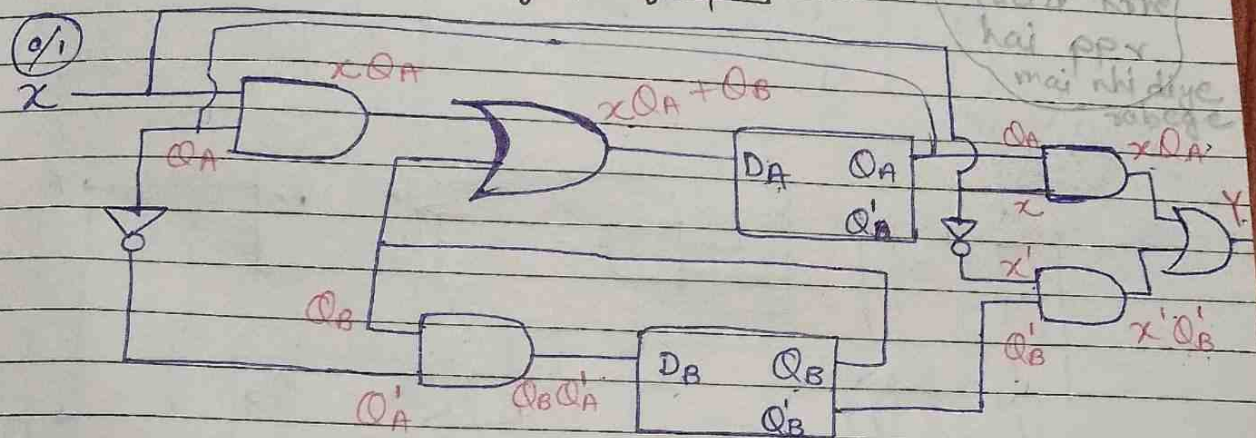Red Pen wale terms  
 Yaad karne hai ppr  
 mai nhi diye



i/p  $\Rightarrow$   $DA = xQA + QB$

$DB = QB \cdot QA'$

$DA = QA^+$   
 $DB = QB^+$

O/p  $\Rightarrow$   $y = xQA + x'QB$

DFF

★ State Table

$Q_A$	$Q_B$	$x$	$D_A$	$D_B$	$Q_A^+$	$Q_B^+$	$y$
0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0
0	1	0	1	1	1	1	0
0	1	1	1	1	1	1	
1	0	0	0				
1	0	1					
1	1	0					
1	1	1					

[Circuit Diagram aagea only]

Circuit aag aa skta hai


Date: \_\_\_\_\_

Page No. \_\_\_\_\_

07/02/23

Confism in qps

★ Analysis with JK flip-flop :-

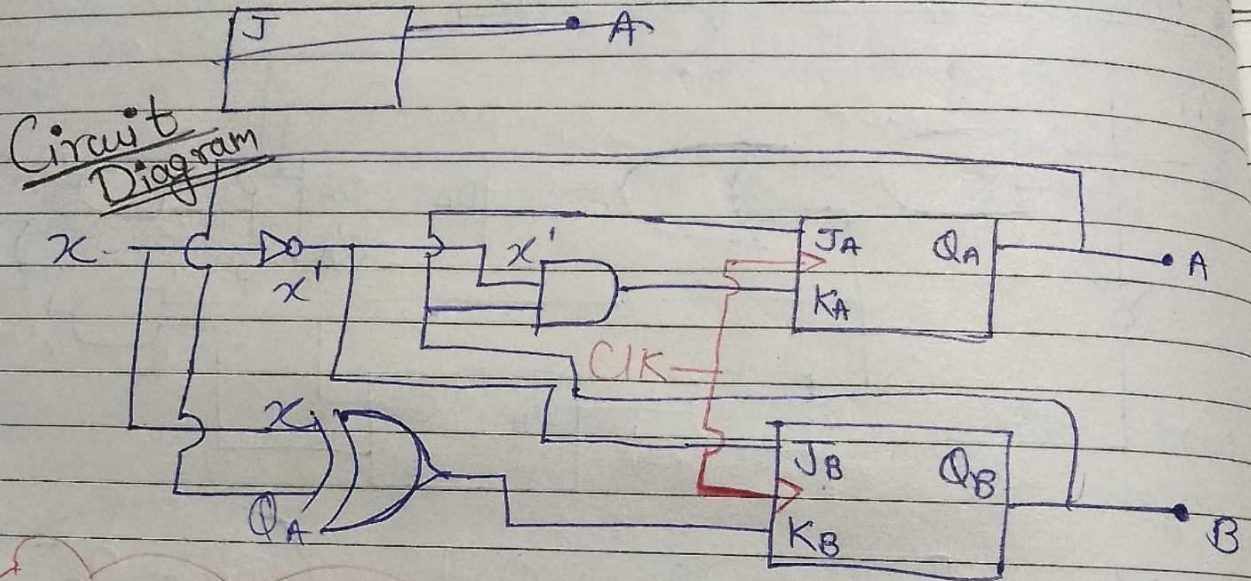

$$J_A = Q_B$$

$$K_A = X' Q_B = K_A = \underline{X' J_A}$$

$$J_B = X'$$

$$K_B = \underline{X \oplus Q_A} = \underline{X' Q_A + X Q_A'}$$




$Q_A^+ / Q_B^+$  Par hi change aayega acc.  
 To flip-flop (Jo bhi flip-flop uke)  
 hisab se


State Table

I/P		x					O/P	
$Q_A$	$Q_B$		$J_A$	$K_A$	$J_B$	$K_B$	$Q_A^+$	$Q_B^+$
0	0	0	0	0	1	0	0	1
0	0	1	0	0	0	1	0	0
0	1	0	1	1	1	0	1	1
0	1	1	1	0	0	1	1	0
1	0	0	0	0	1	1	1	1
1	0	1	0	0	0	0	1	0
1	1	0	1	1	1	1	0	0
1	1	1	1	0	0	0	1	1

★ State Diagram

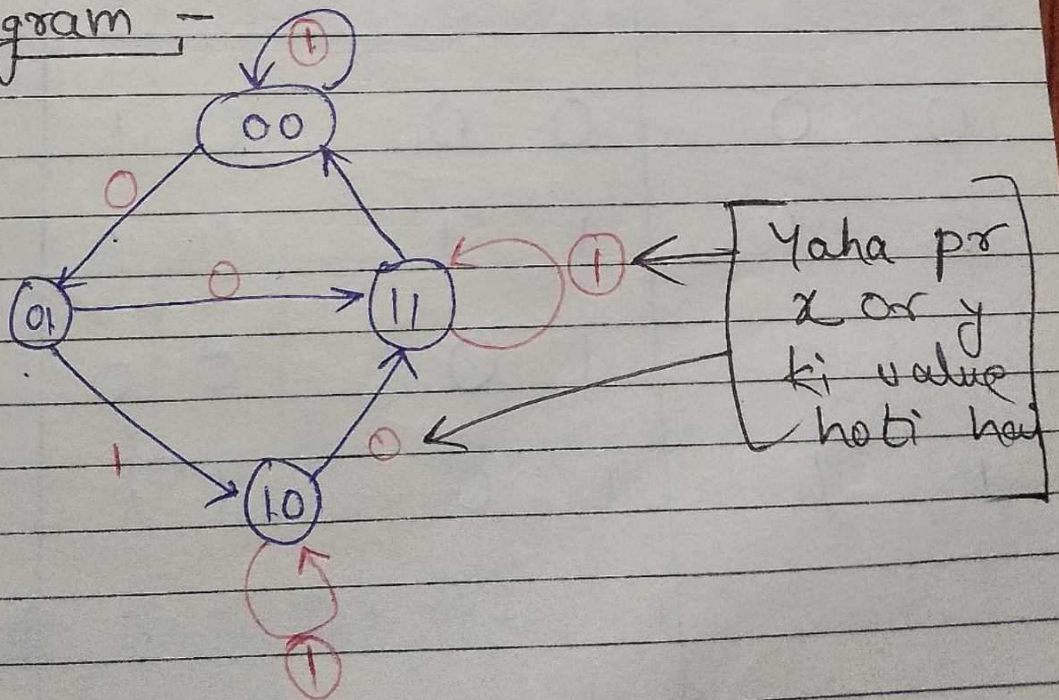

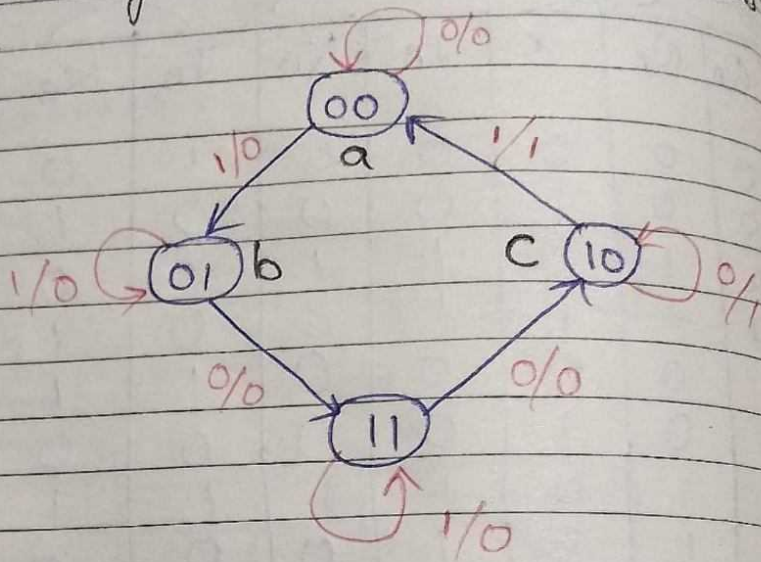Que. Reverse of analysis of sequential circuits



Present State		Next State				O/p (y)	
QA	QB	x=0		x=1		x=0	x=1
		QA <sup>+</sup>	QB <sup>+</sup>	QA <sup>+</sup>	QB <sup>+</sup>		
0	0	0	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	1	0	0	0	1	1
1	1	1	0	1	1	0	0

circuit.

• Find circuit excitation Table -

► Excitation Table -

$Q_A$	$Q_B$	$x$	$Q_A^+$	$Q_B^+$	$T_A$	$T_B$	$y$
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	1	1	0	0
0	1	1	0	1	0	0	0
1	0	0	1	0	0	0	1
1	0	1	0	0	1	0	1
1	1	0	1	0	0	1	0
1	1	1	1	1	0	0	0

$$T_A = Q_A Q_B' x + Q_A Q_B x'$$

$$T_B = Q_A' Q_B' x + Q_A Q_B x'$$

$$y = Q_A Q_B'$$

$T_A$

$x$	$Q_A Q_B$	$Q_A Q_B'$	$Q_A' Q_B$	$Q_A' Q_B'$
$\bar{x}$	0	1	3	1, 2
$x$	4	1, 5	7	6

$$\Rightarrow Q_A Q_B' \bar{x} + Q_A Q_B x$$

$T_B$

$x$	$Q_A Q_B$	$Q_A Q_B'$	$Q_A' Q_B$	$Q_A' Q_B'$
$\bar{x}$	0			
$x$				

[Yaha line se lena hai warna ans. galat aayga]

$T_A$

$Q_A$	$Q_B x$	$Q_B' x$	$Q_B x$	$Q_B' x$
$Q_A$				1
$Q_A$			1	
$Q_A$				